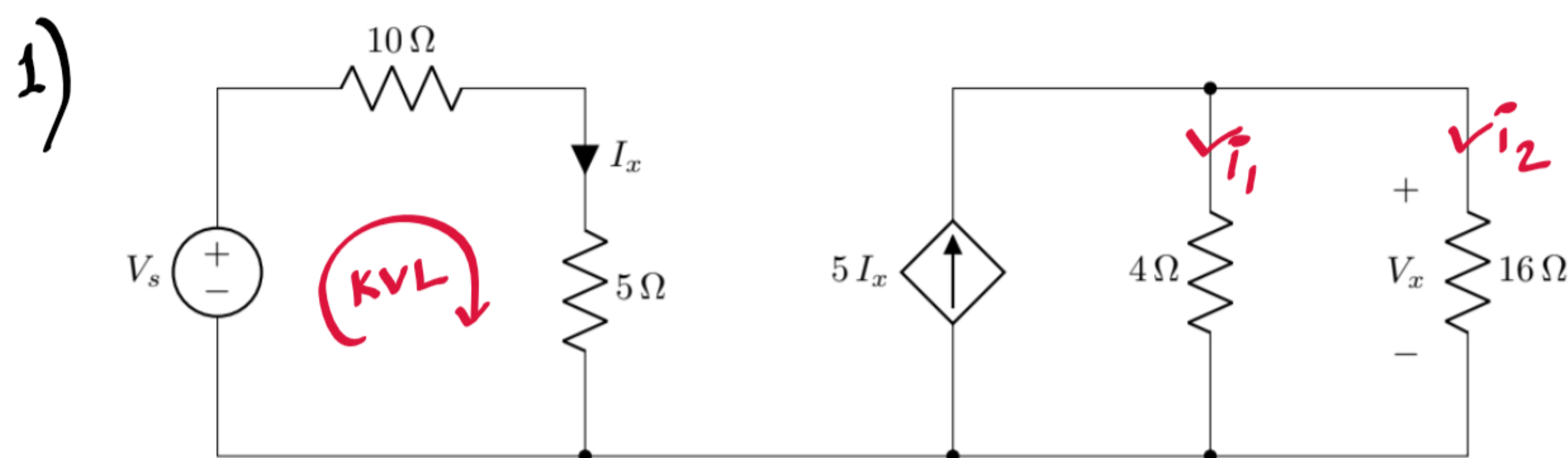


CSE 250 Summer 2015

Set A



a. $P = 16W$

Using $P = V^2/R$,

$\Rightarrow 16 = V_x^2/16$

$\therefore V_x = 16V$

c. KVL in highlighted mesh,

$-V_s + 10I_x + 5I_x = 0$

$[I_x = 1A] \therefore V_s = 15 \times 1$

$= 15V$

b. $5I_x$ divides between 4Ω and 16Ω ;

using CDR,

$i_2 = \frac{R_{eq}}{R_{16}} \times 5I_x$

$\Rightarrow i_2 = \frac{4||16}{16} \times 5I_x$

$= \frac{1}{5} \times 5I_x$

$= I_x$


using Ohm's Law,

$V_x = i_2 \times 16$

$\Rightarrow 16 = i_2 \times 16$

$\therefore i_2 = 1A$

and $I_x = 1A$

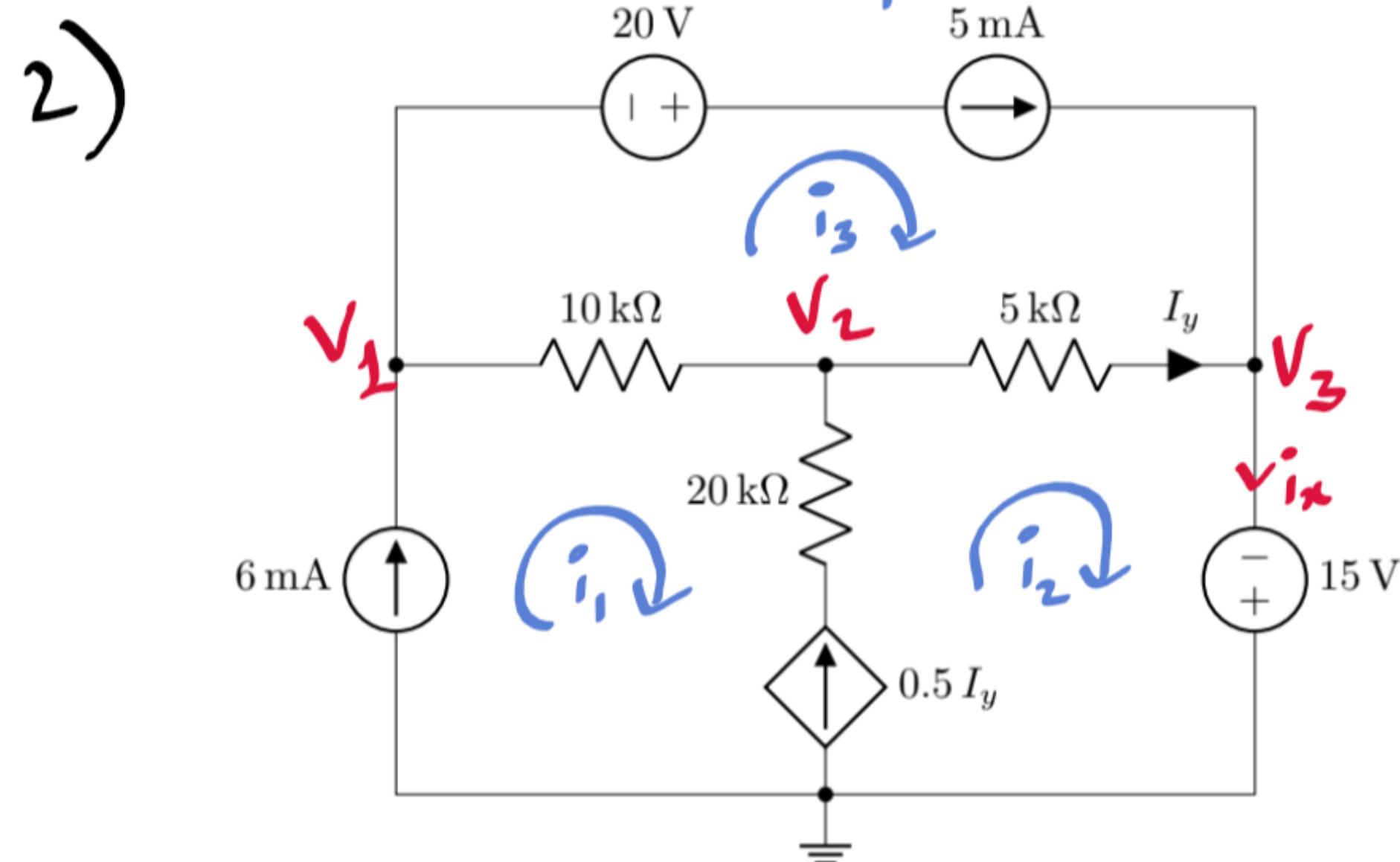

b. see part a).

a. Method 1: Nodal Analysis

$V_1: (-6) + \frac{V_1 - V_2}{10} + 5 = 0$

$\Rightarrow V_1 - V_2 = 10 \text{ --- (i)}$

$V_2: \frac{V_2 - V_1}{10} + (-0.5I_y) + \frac{V_2 - V_3}{5} = 0$

$\Rightarrow -2V_1 + 10V_2 - 2V_3 = I_y \text{ --- (ii)}$

$V_3: V_3 = -15 \text{ --- (iii)}$

$I_y = \frac{V_2 - V_3}{5} \text{ --- (iv)}$

becomes
 $-V_1 + 2V_2 - V_3 = 0$

solving,

$V_1 = 5V, V_2 = -5V, V_3 = -15V$

Method 2: Mesh Analysis

$(1) \downarrow: i_1 = 6 \text{ --- (i)}$ (There is no need to write an equation for mesh 2)

$(3) \downarrow: i_3 = 5 \text{ --- (ii)}$

and KCL equations -

$(2 \text{ and } 3) I_y = i_2 - i_3 \text{ --- (iii)}$

$(1 \text{ and } 2) 0.5I_y = i_2 - i_1 \text{ --- (iv)}$

solve (iv) -

$\therefore i_2 = 7mA$

and $i_1 = 6mA$

$i_3 = 5mA$

becomes
 $-2i_1 + i_2 + i_3 = 0$

i) $P_{5mA} = +5 \times V_n$

$\text{nodal} \left(\begin{aligned} &= 5 \times (V_1 - V_3 + 20) \\ &= 200mW \\ &\text{(absorbed)} \end{aligned} \right.$






$\text{mesh} \left(\begin{aligned} &= +5 [20 - 5(i_3 - i_2) - 10(i_3 - i_1)] \\ &= 200mW \\ &\text{(absorbed)} \end{aligned} \right.$

ii) $P_{15V} = -i_x \times 15$

$\text{nodal} \left(\begin{aligned} &= -(5 + I_y) \times 15 \\ &= -105mW \\ &\text{(supplied)} \end{aligned} \right.$

$\text{mesh} \left(\begin{aligned} &= -i_2 \times 15 \\ &= -105mW \\ &\text{(supplied)} \end{aligned} \right.$

3)

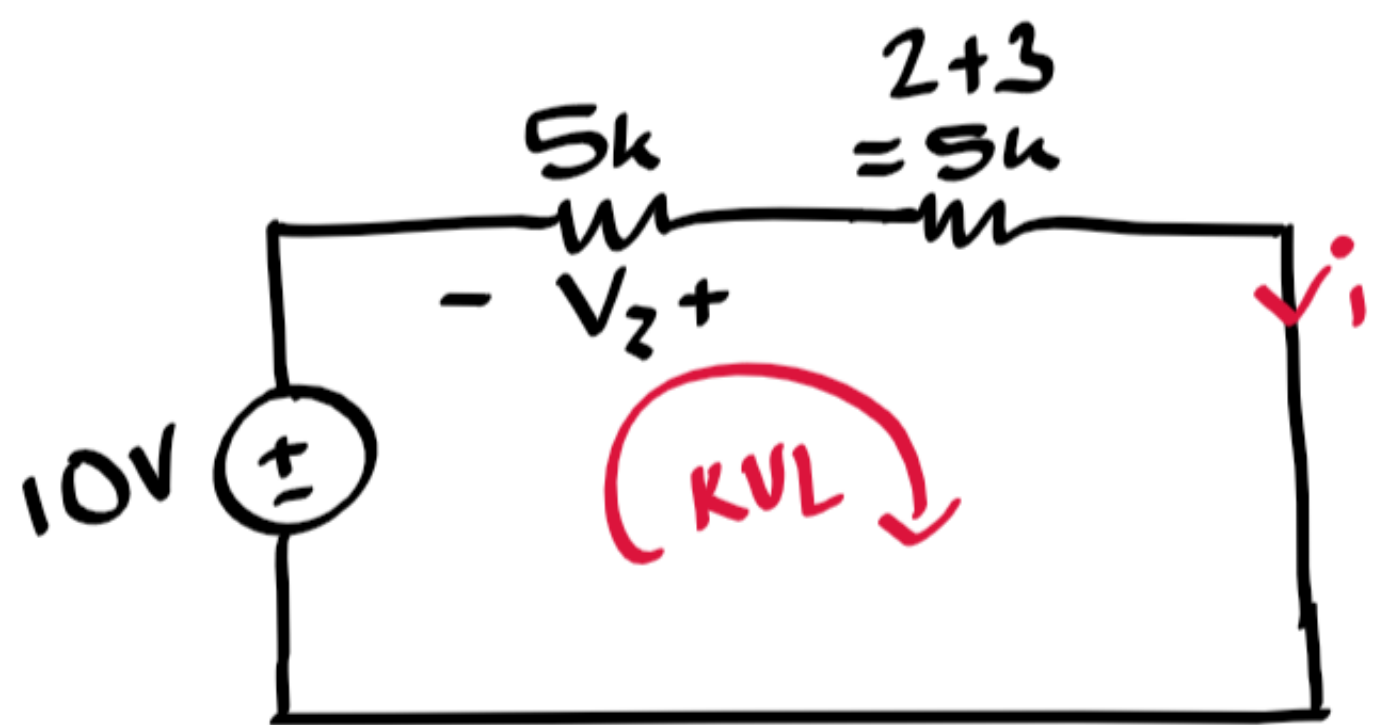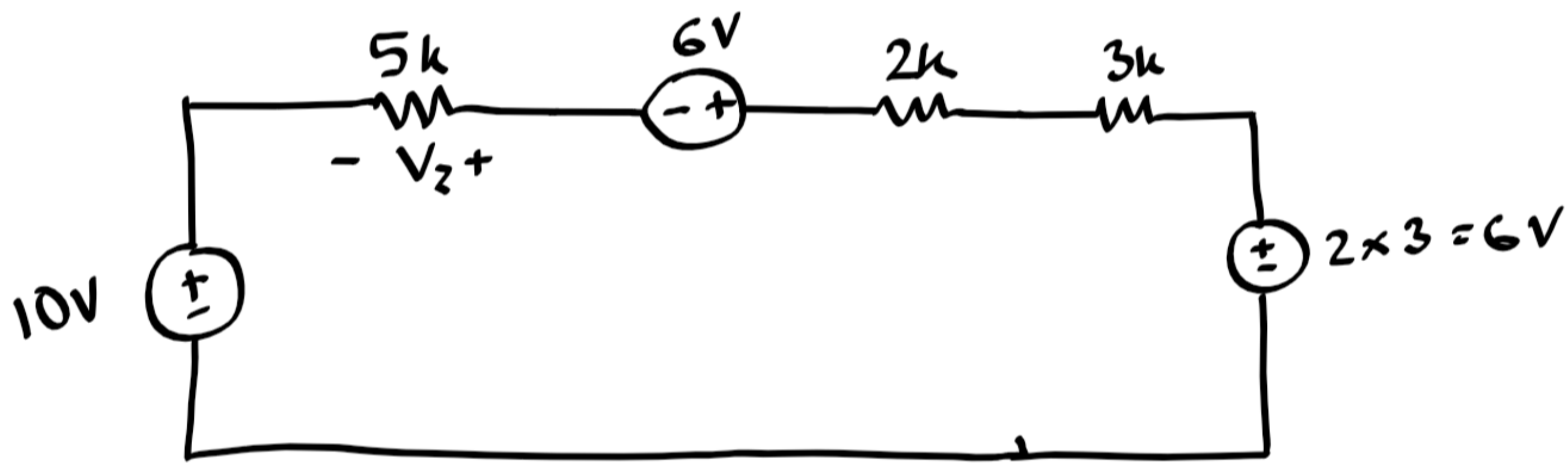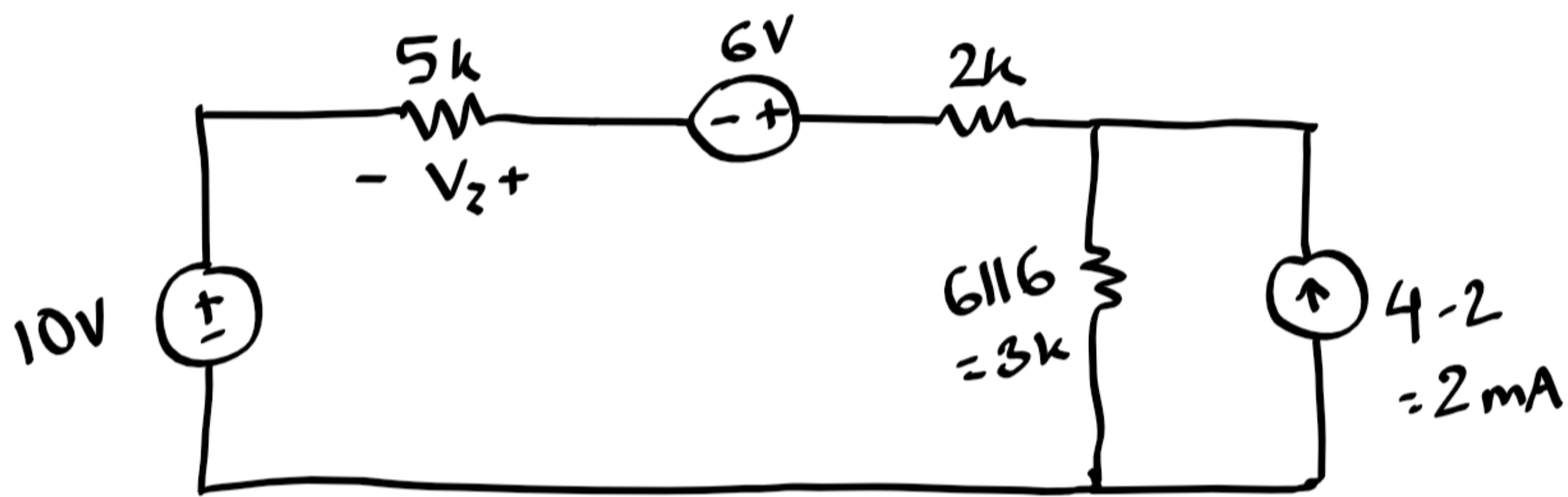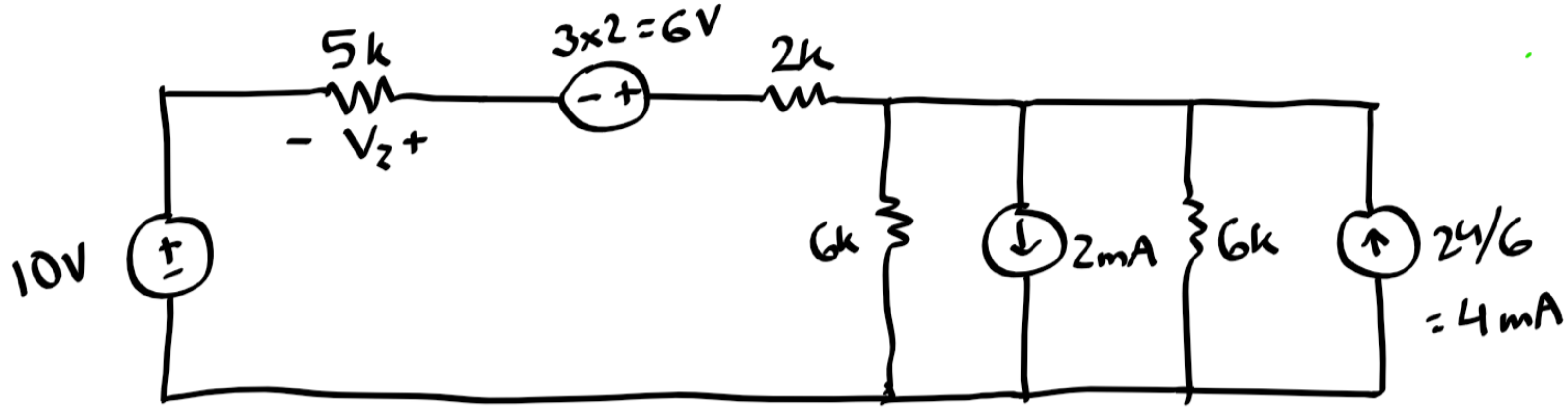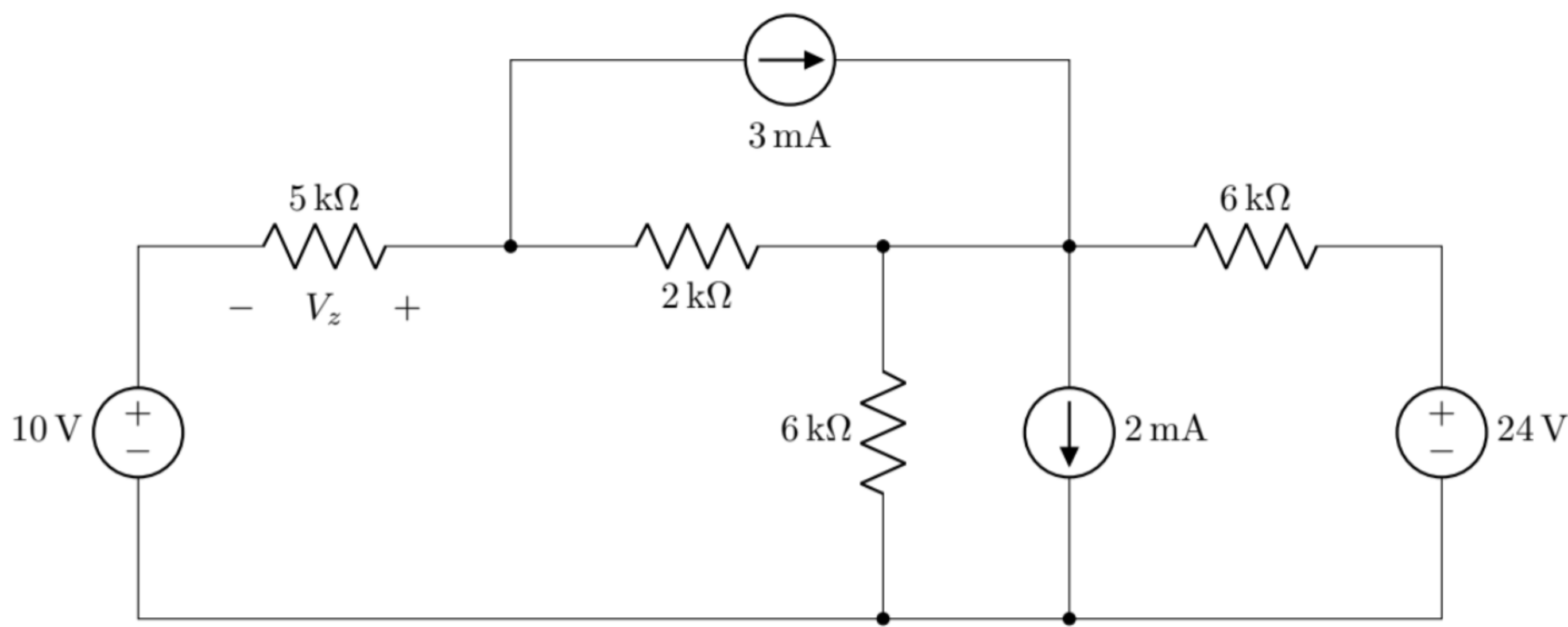


KVL ,
 $-10 + 5i + 5i = 0$
 $i = 1 \text{ mA}$
 $\therefore V_z = -5i$
 $= -5 \text{ V}$


or

VDR,
 $V_z = -\frac{5}{5+5} \times 10$
 $= -5 \text{ V}$


4) ∞.

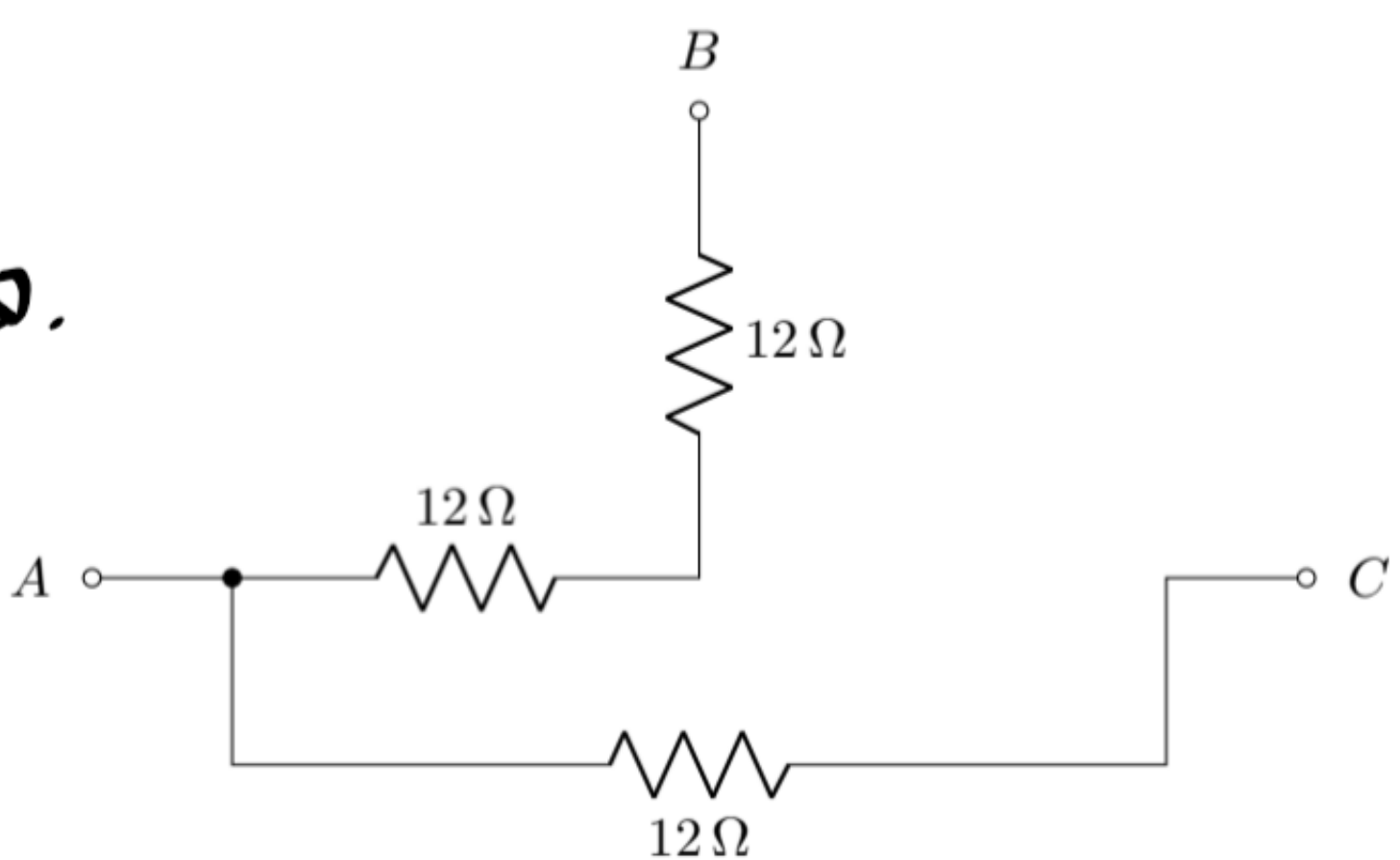

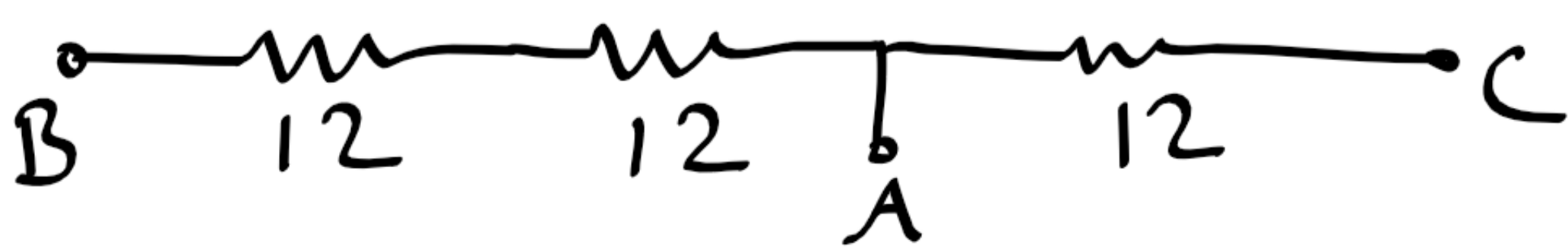For ease of visualization,
 straighten out the configuration-



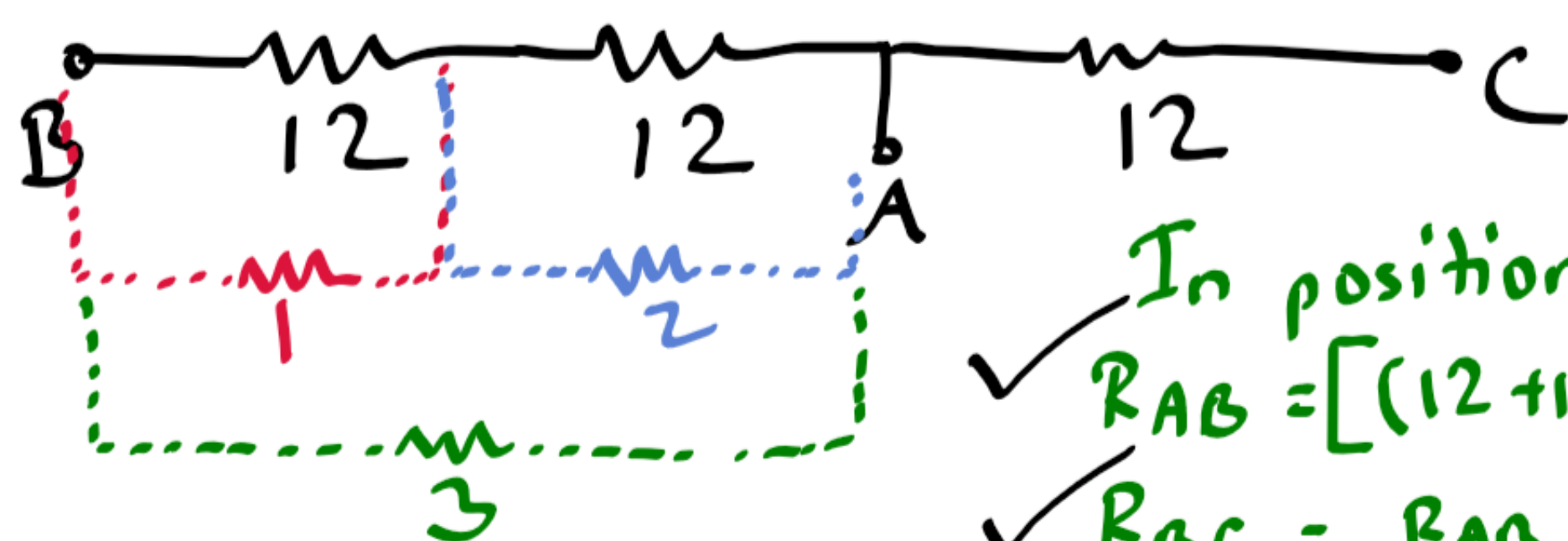
Connecting the new resistor across nodes A-C would change the given $R_{AC} = 12 \Omega$, so the resistor connected would have to be in any one of the following positions-







In position 3,
 $R_{AB} = [(12+12) \parallel 12] = 8$
 $R_{BC} = R_{AB} + 12 = 20$

In position 1,
 $R_{AB} = (12 \parallel 12) + 12 = 18$

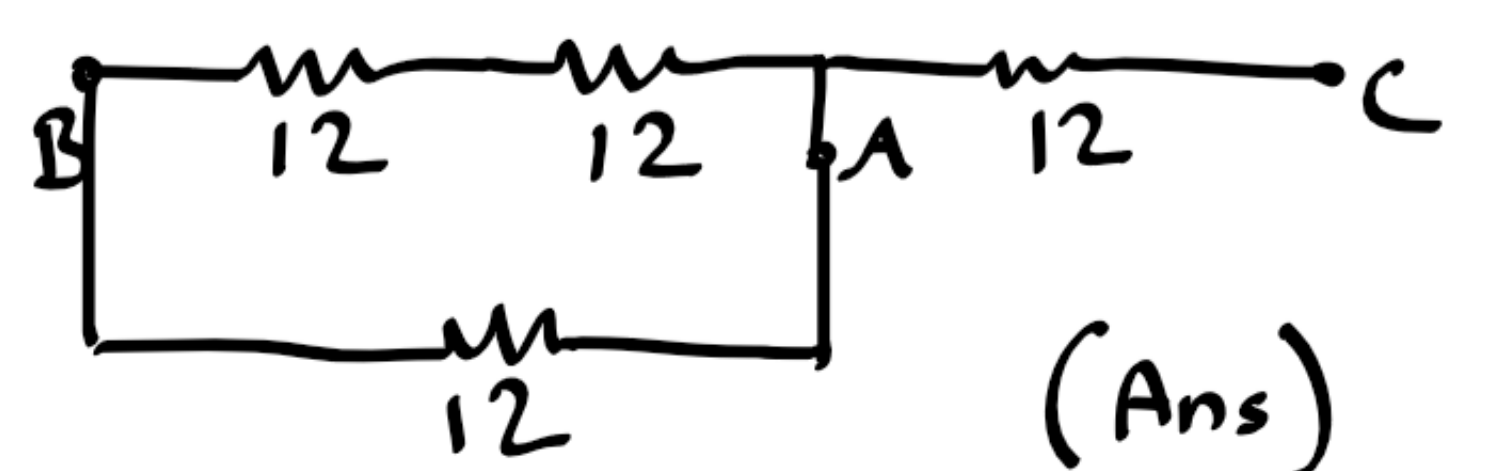In position 2,
 $R_{AB} = 12 + (12 \parallel 12) = 18$




4) b.

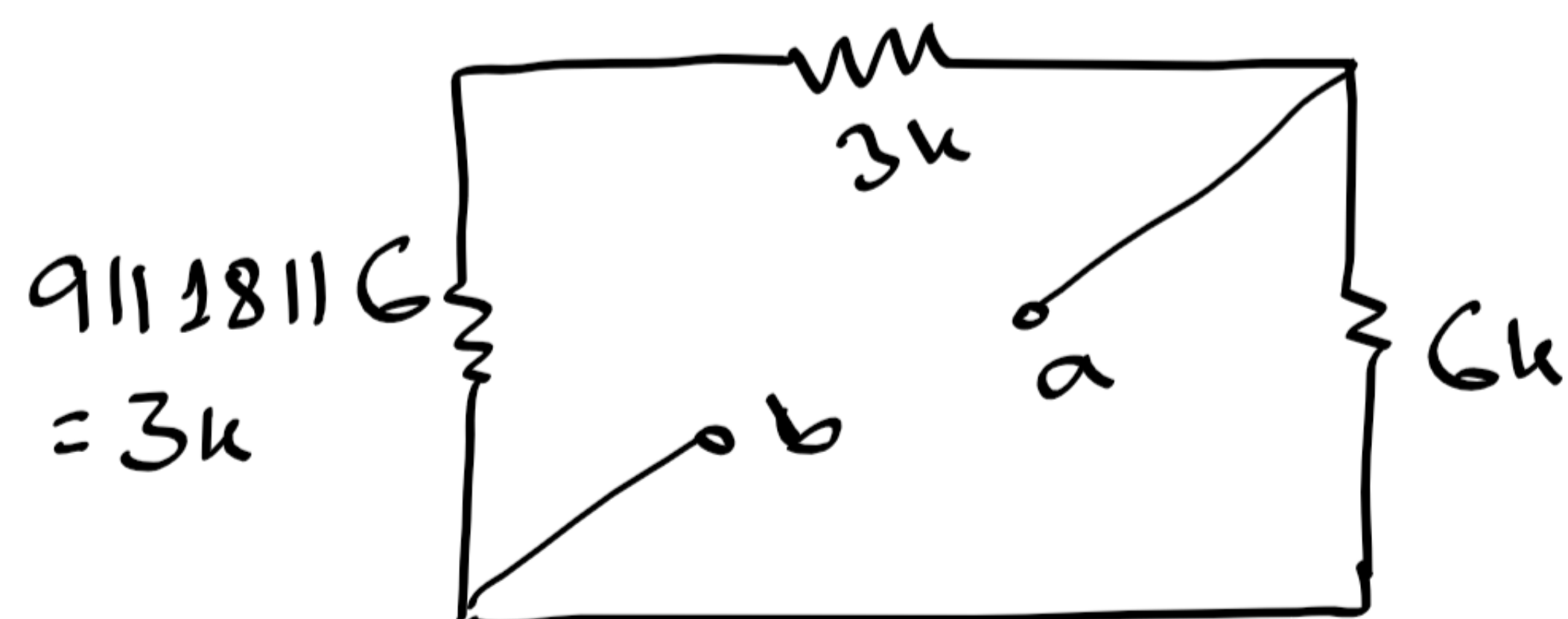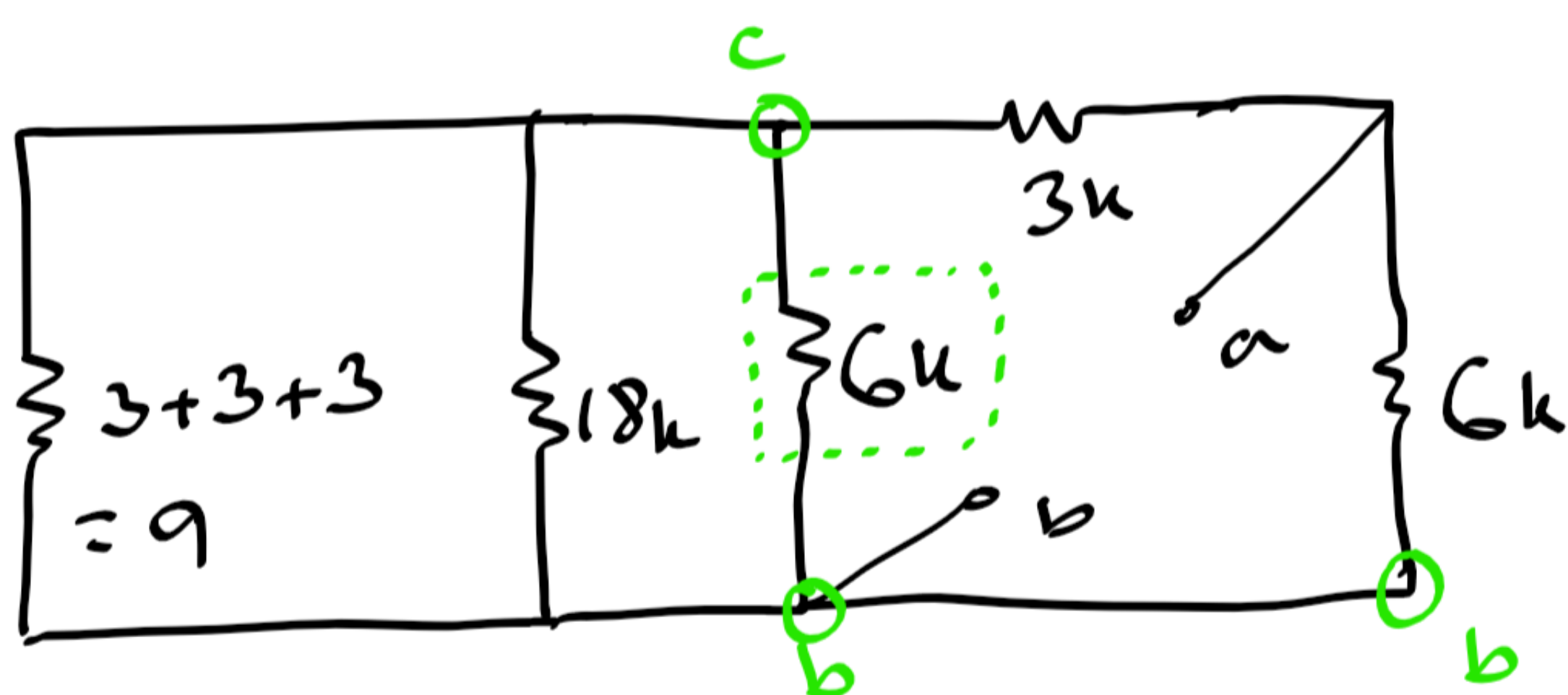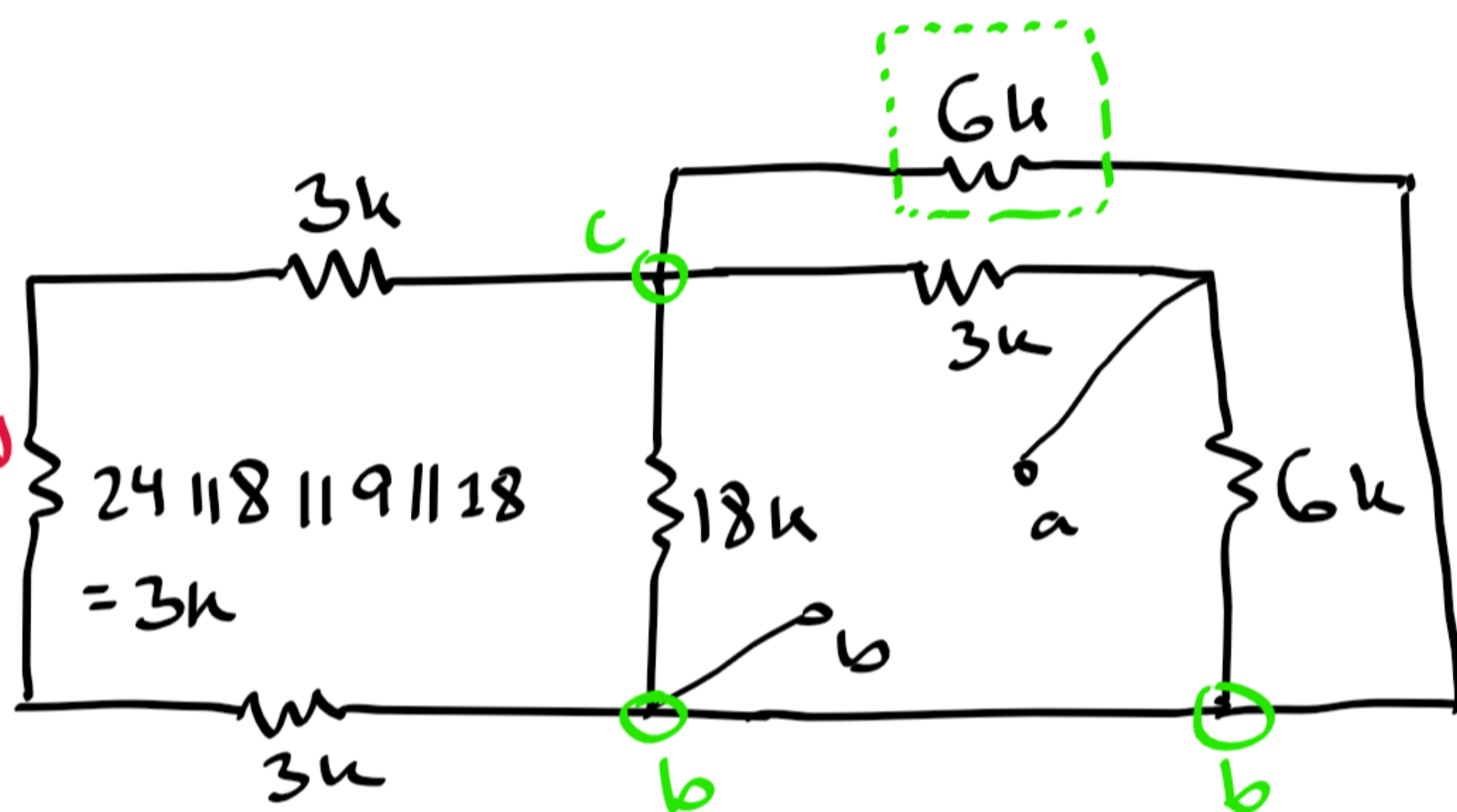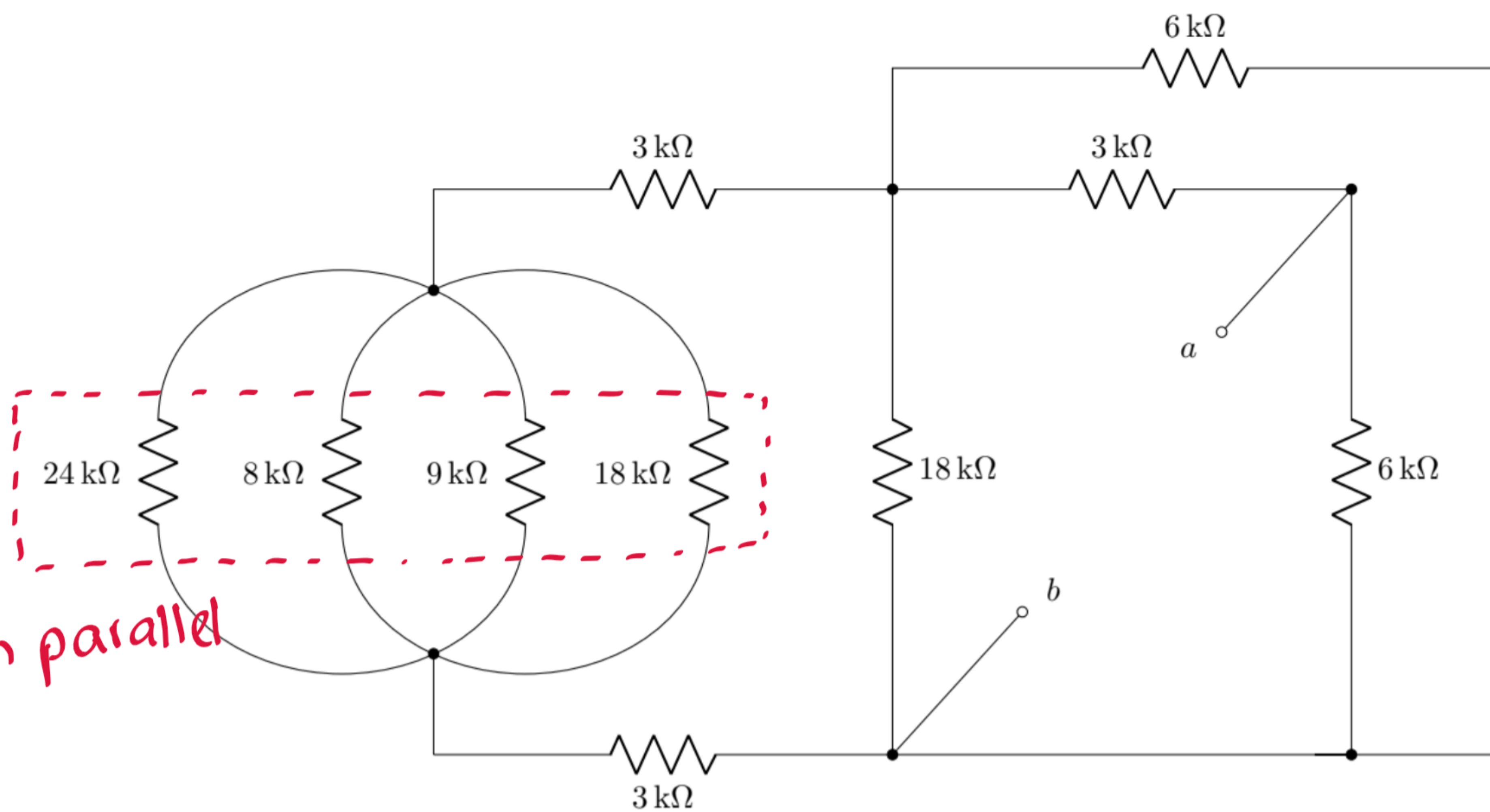

$$\therefore R_{ab} = (3+3) \parallel 6 = 3 \text{ k}\Omega$$

Set B

1)

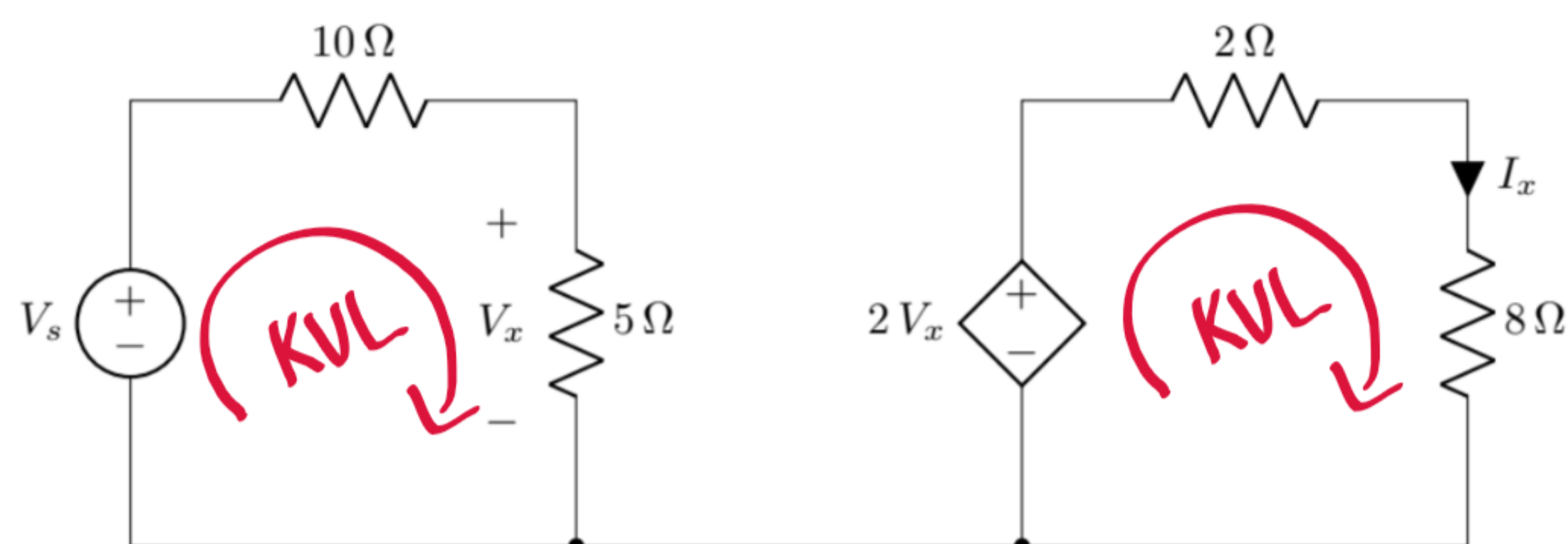

a. $P = 8 \text{ W}$

Using $P = I^2 R$,

$\Rightarrow 8 = I_x^2 \times 8$

$\therefore I_x = 1 \text{ A}$

c. Apply VDR in left mesh,

$\Rightarrow V_x = \frac{5}{5+10} \times V_s$

$\therefore V_s = 15 \text{ V}$

b. KVL in right mesh,

$-2V_x + 2I_x + 8I_x = 0$

$\therefore V_x = 5 \text{ V}$


or use VDR,

$V_{8\Omega} = \frac{8}{2+8} \times 2V_x$

$\Rightarrow 8I_x = \frac{8}{10} \times 2V_x$

$\Rightarrow V_x = 5 \text{ V}$

2)

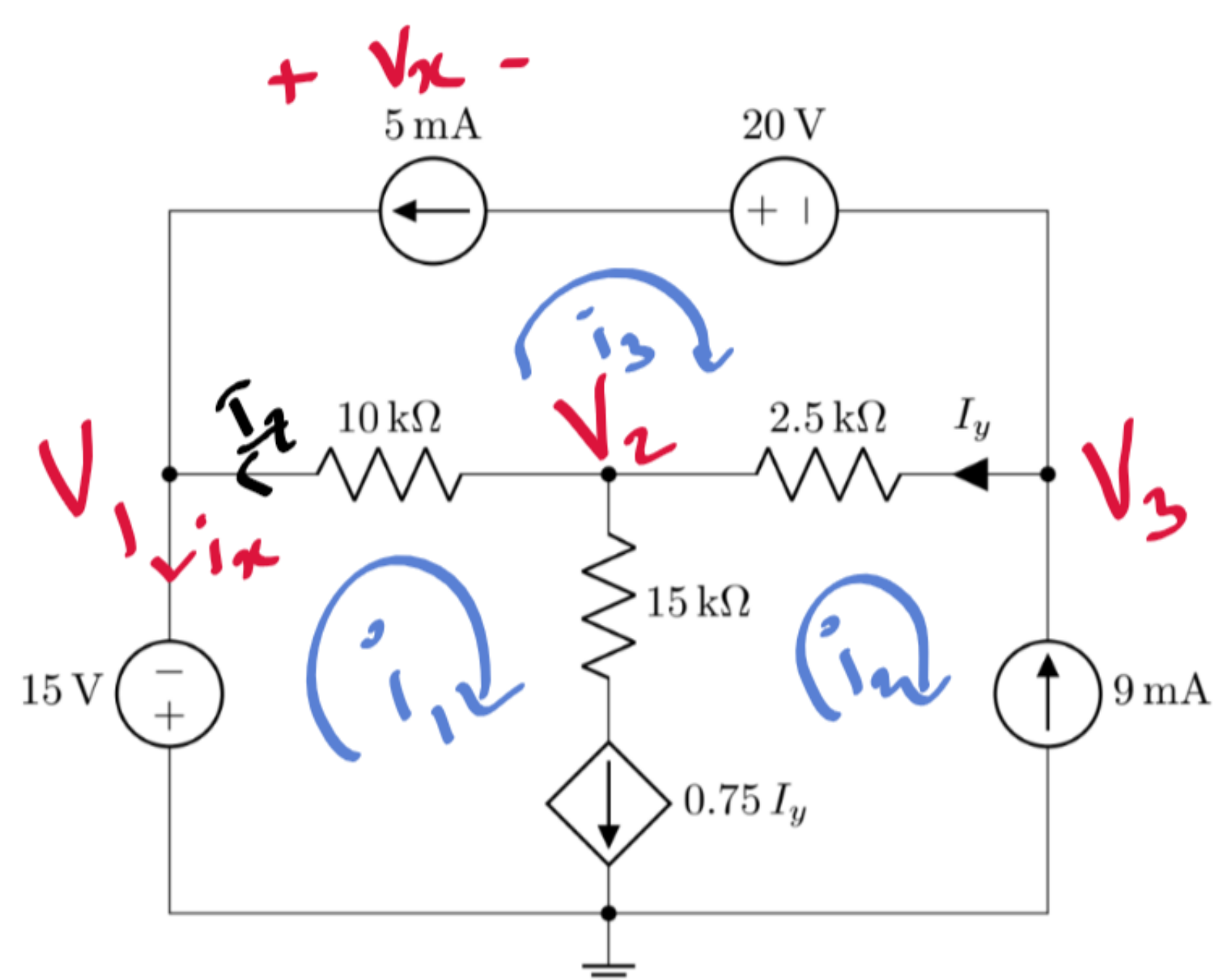

b. see part a).

a. Method 1 : Nodal Analysis

$V_1 : V_1 = -15 \text{ — (i)}$

$V_2 : \frac{V_2 - V_1}{10} + 0.75 I_y + \frac{V_2 - V_3}{2.5} = 0$

$\Rightarrow -2V_1 + 10V_2 - 8V_3 = 15 I_y \text{ — (ii)}$

$V_3 : (-9) + \frac{V_3 - V_2}{2.5} + 5 = 0$

$\Rightarrow V_3 - V_2 = 10 \text{ — (iii)}$

$I_y = \frac{V_3 - V_2}{2.5} \text{ — (iv)}$

solving,

$V_1 = -15 \text{ V}, V_2 = -5 \text{ V}, V_3 = 5 \text{ V}$

Method 2 : Mesh Analysis

$(2) : i_2 = -9 \text{ — (i)}$ (There is no need to write an equation for mesh 1)

$(3) : i_3 = -5 \text{ — (ii)}$

and KCL equations -

$(3 \text{ and } 2) I_y = i_3 - i_2 \text{ — (iii)}$

$(1 \text{ and } 2) 0.75 I_y = i_1 - i_2 \text{ — (iv)}$

solve (iv) -

$\therefore i_1 = -6 \text{ mA}$

and $i_2 = -9 \text{ mA}$

$i_3 = -5 \text{ mA}$

becomes $4i_1 - i_2 - 3i_3 = 0$

i) $P_{5\text{mA}} = -5 \times V_x$

nodal $= -5 \times (V_1 - V_3 - 20)$
 $= 200 \text{ mW}$
(absorbed)

mesh $= -5 [-20 - 10(i_3 - i_1) - 2.5(i_3 - i_2)]$
 $= 200 \text{ mW}$
(absorbed)






ii) $P_{15\text{V}} = -i_x \times 15$

nodal $= -(5 + I_x) \times 15$
 $= -90 \text{ mW}$
(supplied)

mesh $= -(-i_1) \times 15$
 $= -90 \text{ mW}$
(supplied)

$I_x = \frac{V_2 - V_1}{10}$

3)

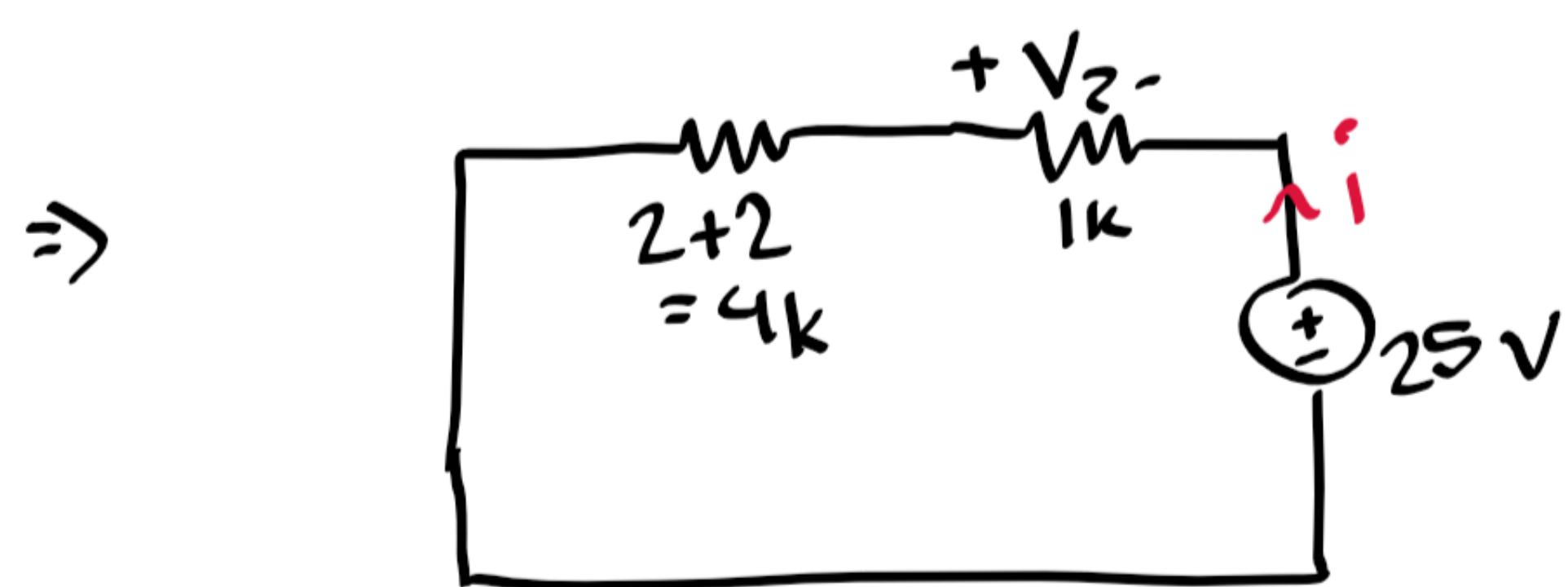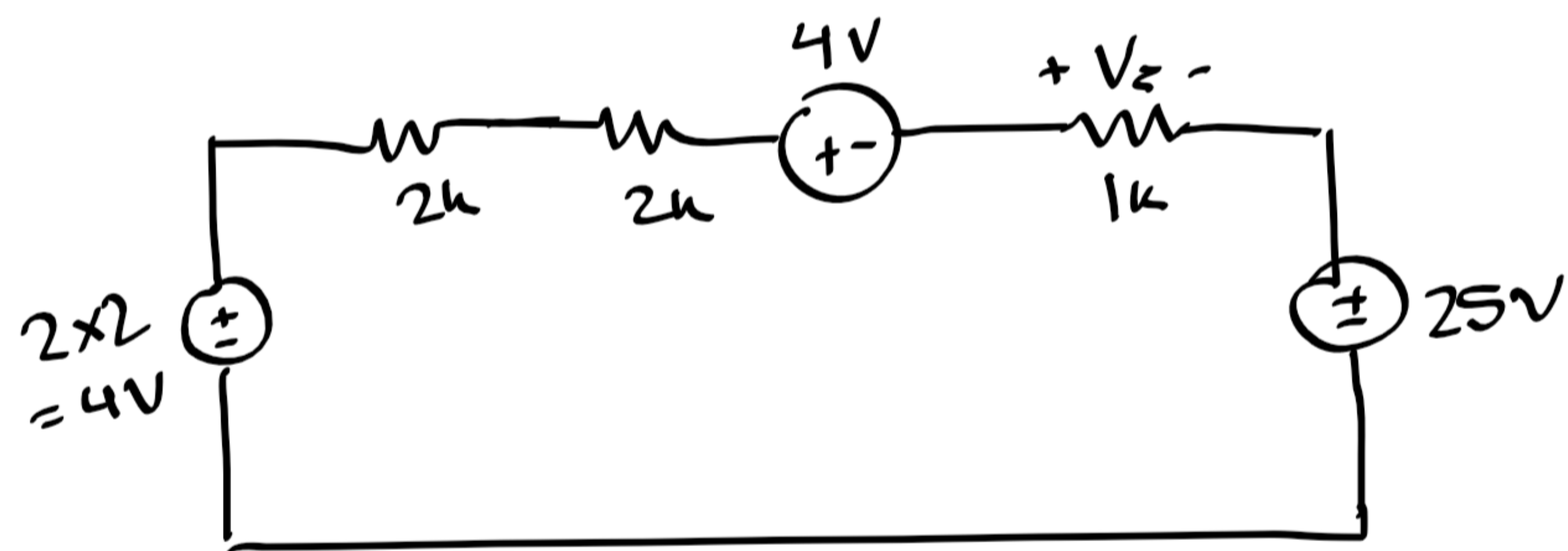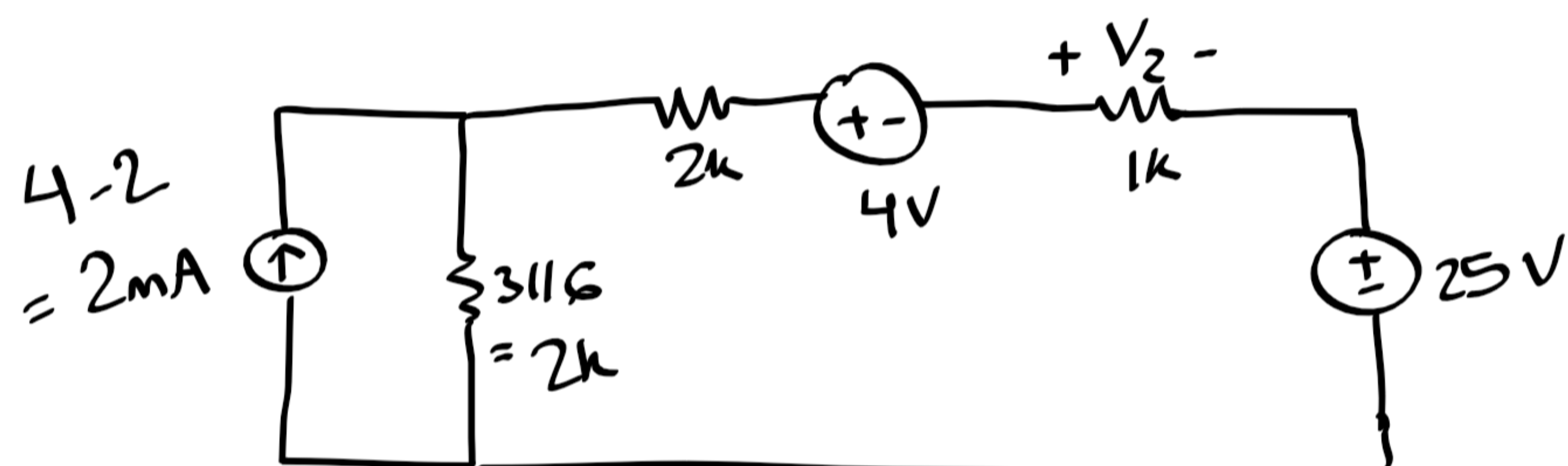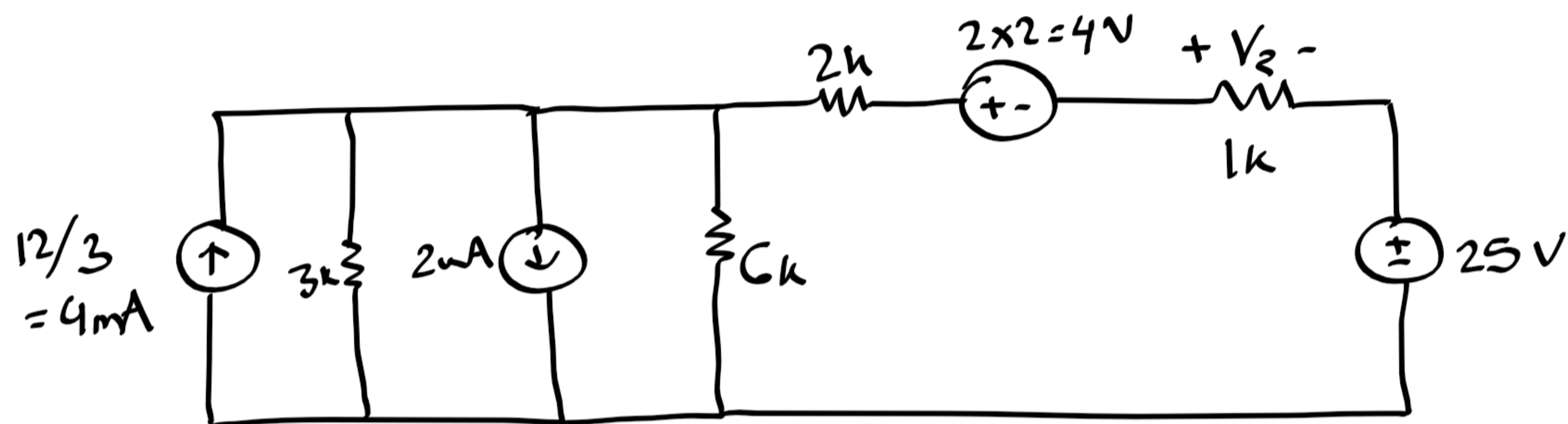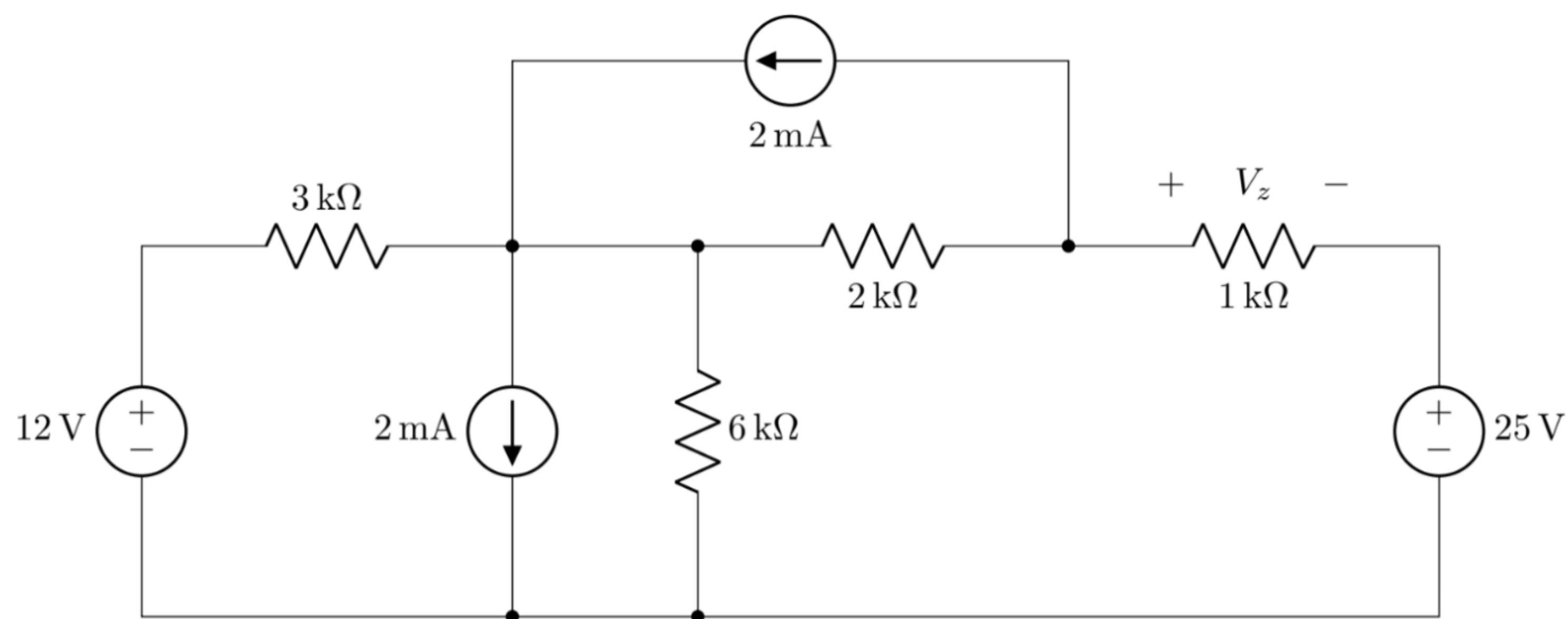

KVL ,
 $-4i - 1i + 25 = 0$
 $i = 5\text{mA}$
 $\therefore V_z = -1i$
 $= -5\text{V}$





or

VDR,
 $V_z = -\frac{1}{1+4} \times 25$
 $= -5\text{V}$

4) a. same as set A.

(nodes A and C have been interchanged)

4) b.

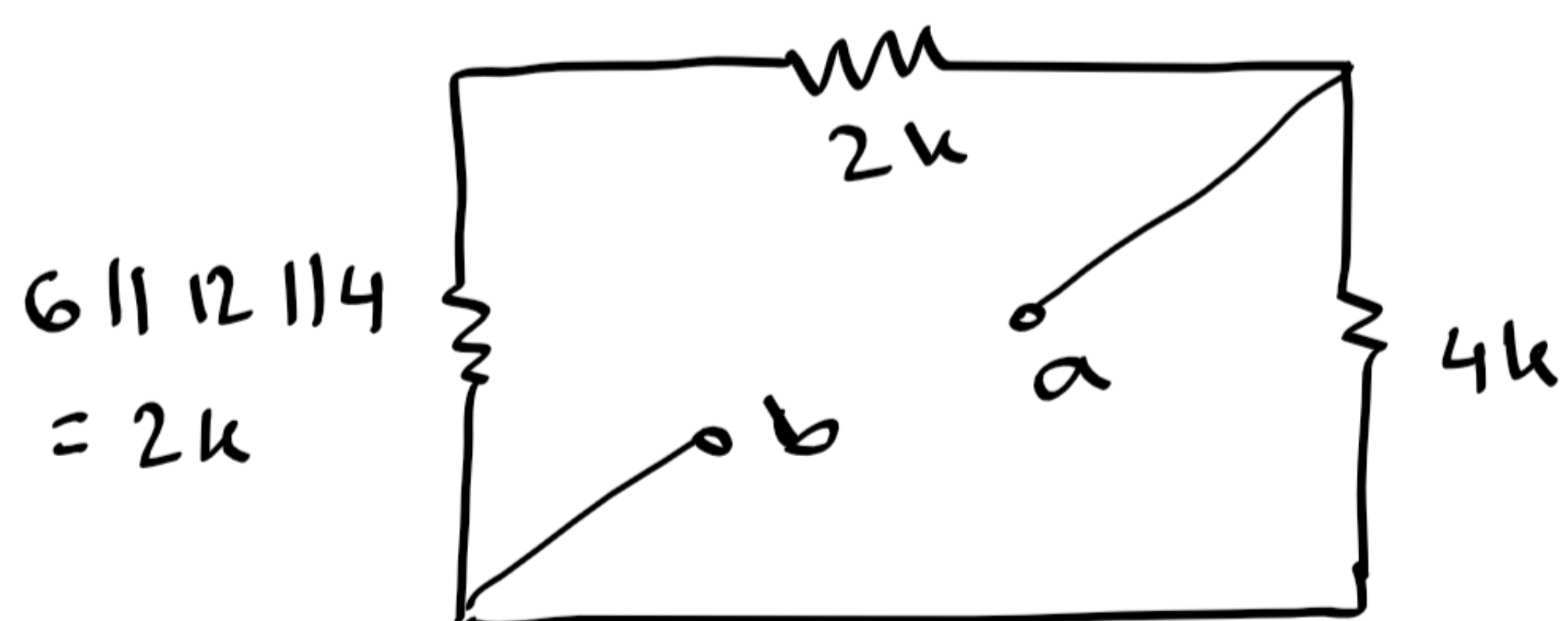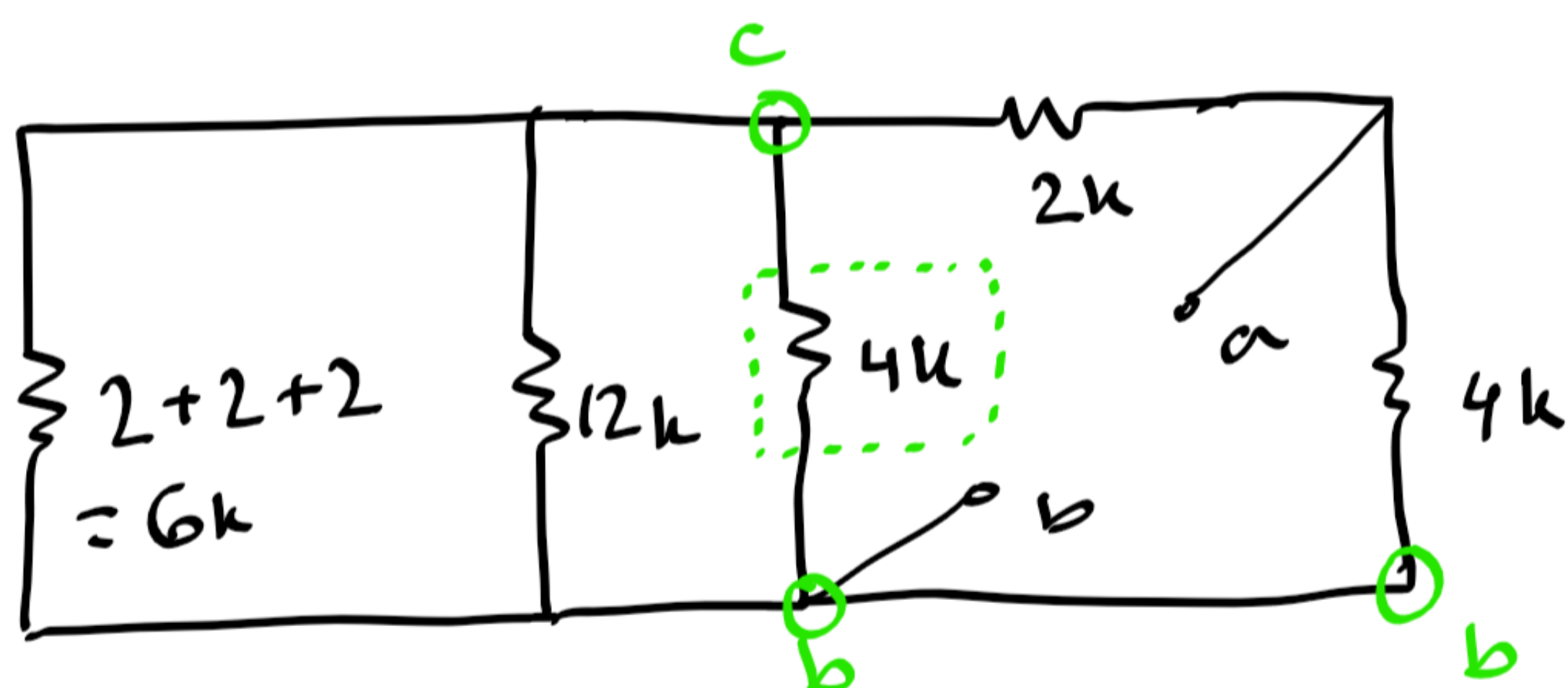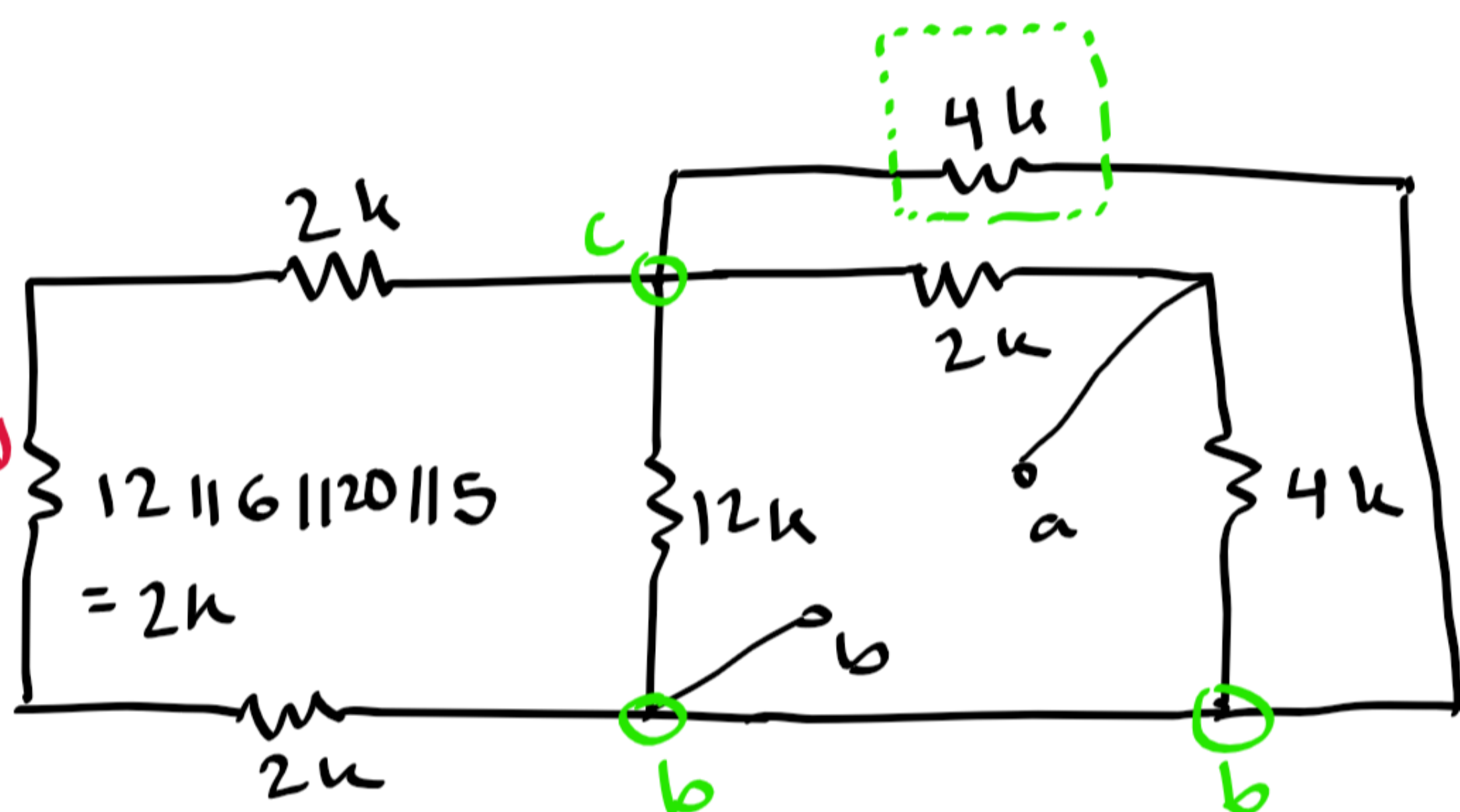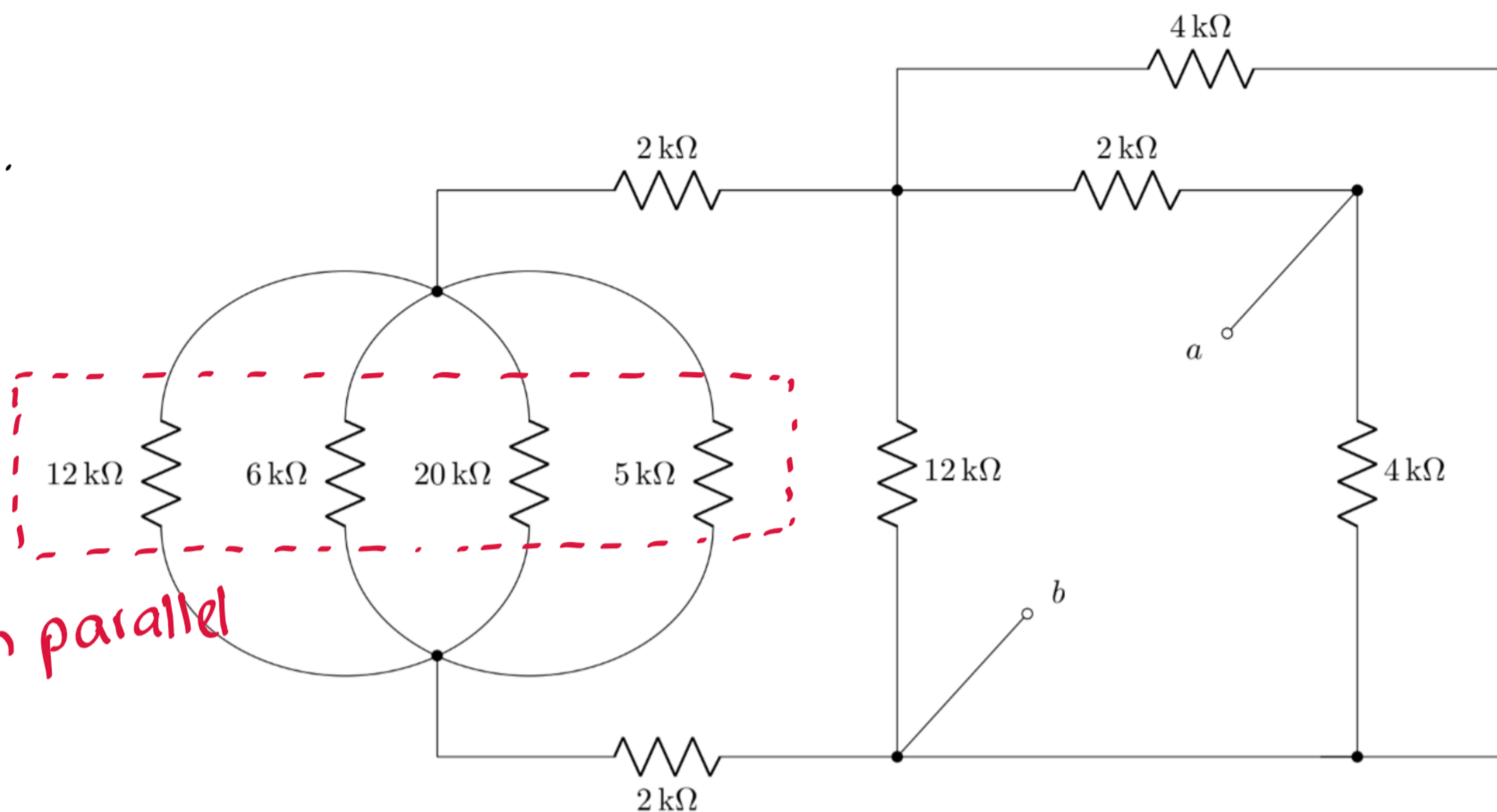

$$\therefore R_{ab} = (2+2) \parallel 4 = 2k\Omega$$